

Lecture 07 08 09

Pipeline Processor with Hazard

Jun WANG

Contents

- ISA (instruction set architecture)
 - Operation field
 - Storage and access
 - Operations
- MA (micro architecture)
 - Top-view and block diagram
 - Verilog for stages
- Hazard in MA

Design target

- RISC CPU
- Data path 16b
- Data memory
 - $2^8 \times 16b$
- Operation memory:
 - $2^8 \times 16b$
 - Size of operation set: 2^5
- General register
 - $8 \times 16b$
- Flags
 - NF, ZF, CF
- Control
 - Clock, reset, enable, start
- Testing
 - 4 bit selection for 16 bit output

Operation field

				15	11	10	8	7	4	3	0
				Op code (5 bit)		Operand 1 (3 bit)		Operand 2 (4 bit)		Operand 3 (4 bit)	
						<i>r1</i>		<i>r2</i>		<i>r3</i>	
R type (register type)	<i>r1</i>	<i>r2</i>	<i>r3</i>	000: gr[0]		x000: gr[0]		x000: gr[0]			
				001: gr[1]		x001: gr[1]		x001: gr[1]			
				010: gr[2]		x010: gr[2]		x010: gr[2]			
				011: gr[3]		x011: gr[3]		x011: gr[3]			
				100: gr[4]		x100: gr[4]		x100: gr[4]			
I type (Immediate type)	<i>r1</i>	val2	val3	101: gr[5]		x101: gr[5]		x101: gr[5]			
				110: gr[6]		x110: gr[6]		x110: gr[6]			
				111: gr[7]		x111: gr[7]		x111: gr[7]			
RI type	<i>r1</i>	<i>r2</i>	val3					<i>val2</i>		<i>val3</i>	
								Immediate data (4 bit)		Immediate data (4 bit)	

gr: general register
(16 bit X 8)

Access memory and register

- Access register:
 - Ex. $gr[r1]$,
 - $r1$ for simplification
 - $[r1]/r1$ gets register number
- Access memory:
 - Ex. $m[r2+val3]$,
 - $[r2+val3]/[gr(r2)+val3]$ gets address of memory
- Access immediate data:
 - Ex. $\{val2, val3\}$,
 - MSB: $val2$, LSB: $val3$

An example of operation codes (assembly language)

- LOAD gr1, gr0, 0
- LOAD gr2, gr0, 1
- NOP
- NOP
- NOP
- ADD gr3, gr1, gr2
- NOP
- NOP
- NOP
- STORE gr3, gr0, 2
- HALT

In C code:

$Y = A + B$

$M[\text{gr0}+2] = M[\text{gr0}+1] + M[\text{gr0}+0]$

Operation

- Data transfer & Arithmetic

mnemonic	operand1	operand2	operand3	op code	operation
NOP *				00000	no operation
HALT *				00001	halt
LOAD *	r1	r2	val3	00010	$gr[r1] \leftarrow m[r2+val3]$
STORE *	r1	r2	val3	00011	$m[r2+val3] \leftarrow r1$
LDIH	r1	val2	val3	10000	$r1 \leftarrow r1 + \{val2, val3, 0000_0000\}$ (lower 8'b0 can be given with ADDI)
ADD *	r1	r2	r3	01000	$r1 \leftarrow r2 + r3$
ADDI	r1	val2	val3	01001	$r1 \leftarrow r1 + \{val2, val3\}$
ADDC	r1	r2	r3	10001	$r1 \leftarrow r2 + r3 + CF$
SUB	...				
SUBI	...				
SUBC	...				
CMP *		r2	r3	01100	$r2 - r3$; set CF, ZF and NF

Operation

- Logical / shift

mnemonic	operand 1	operand2	operand3	op code	operation
AND	r1	r2	r3	01101	r1<-r2 and r3
OR	...				
XOR	...				
SLL	r1	r2	val3	00100	r1<-r2 shift left logical (val3 bit shift)
SRL	...				
SLA	r1	r2	val3	00101	r1<-r2 shift left arithmetical (val3 bit shift)
SRA	...				

Logical shift: 1001 SRL 2b → 0010 (append 0)

Arithmetical shift: 1001 SRA 2b → 1110 (keep the sign)

Operation

- Control


Flag registers:

- Used for control operations (conditional branch)
- ZF (zero flag), NF (negative flag), CF (carry flag)


mnemonic	operand 1	operand2	operand3	op code	operation
JUMP		val2	val3	11000	jump to {val2, val3}
JMPR	r1	val2	val3	11001	jump to r1+{val2, val3}
BZ	r1	val2	val3	11010	if ZF=1 branch to r1+{val2, val3}
BNZ	r1	val2	val3	11011	if ZF=0 branch to r1+{val2, val3}
BN	r1	val2	val3	11100	if NF=1 branch to r1+{val2, val3}
BNN	...				
BC	r1	val2	val3	11110	if CF=1 branch to r1+{val2, val3}
BNC	...				

Block diagram

smdr: data for
save memory
directly

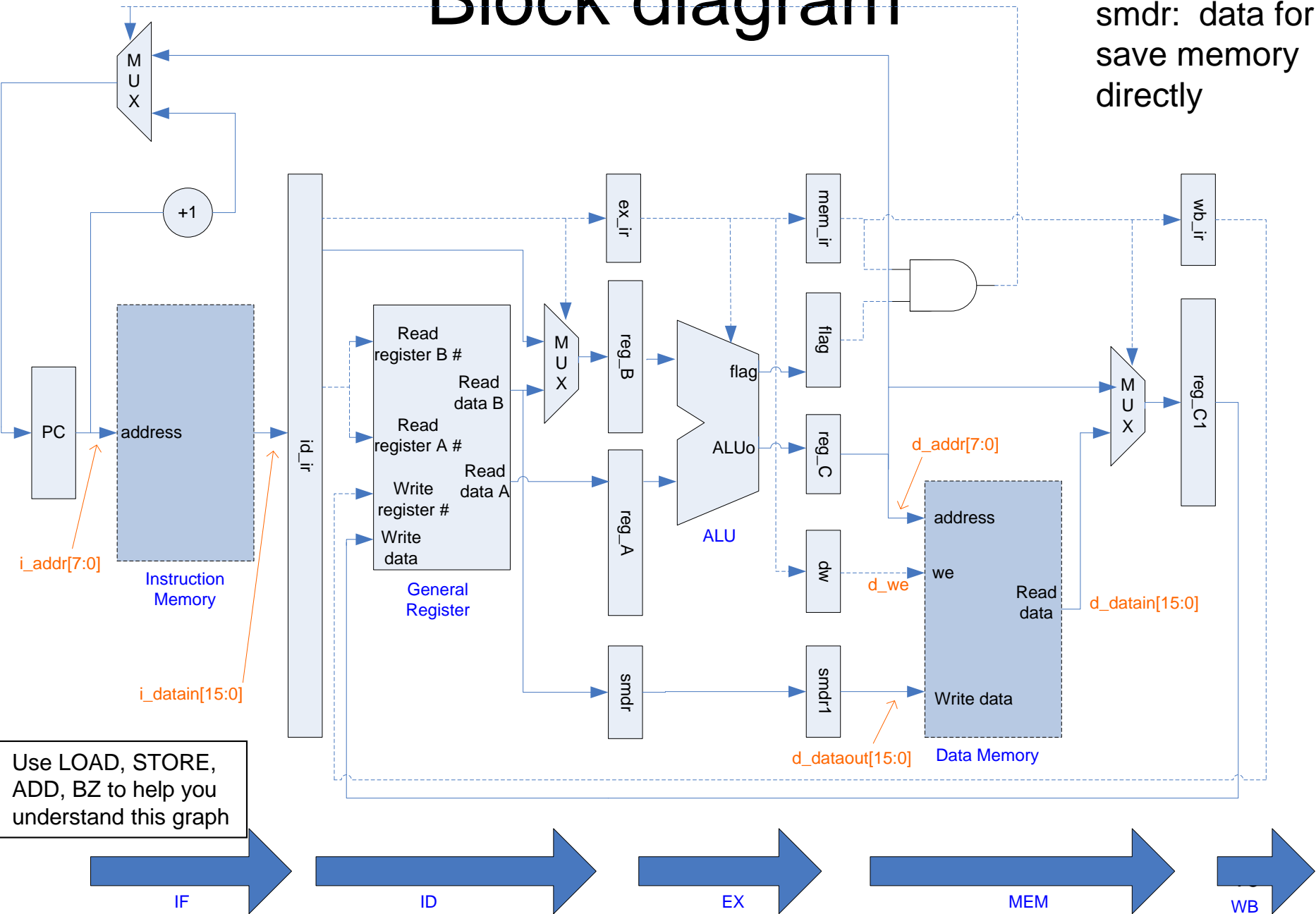


Top view

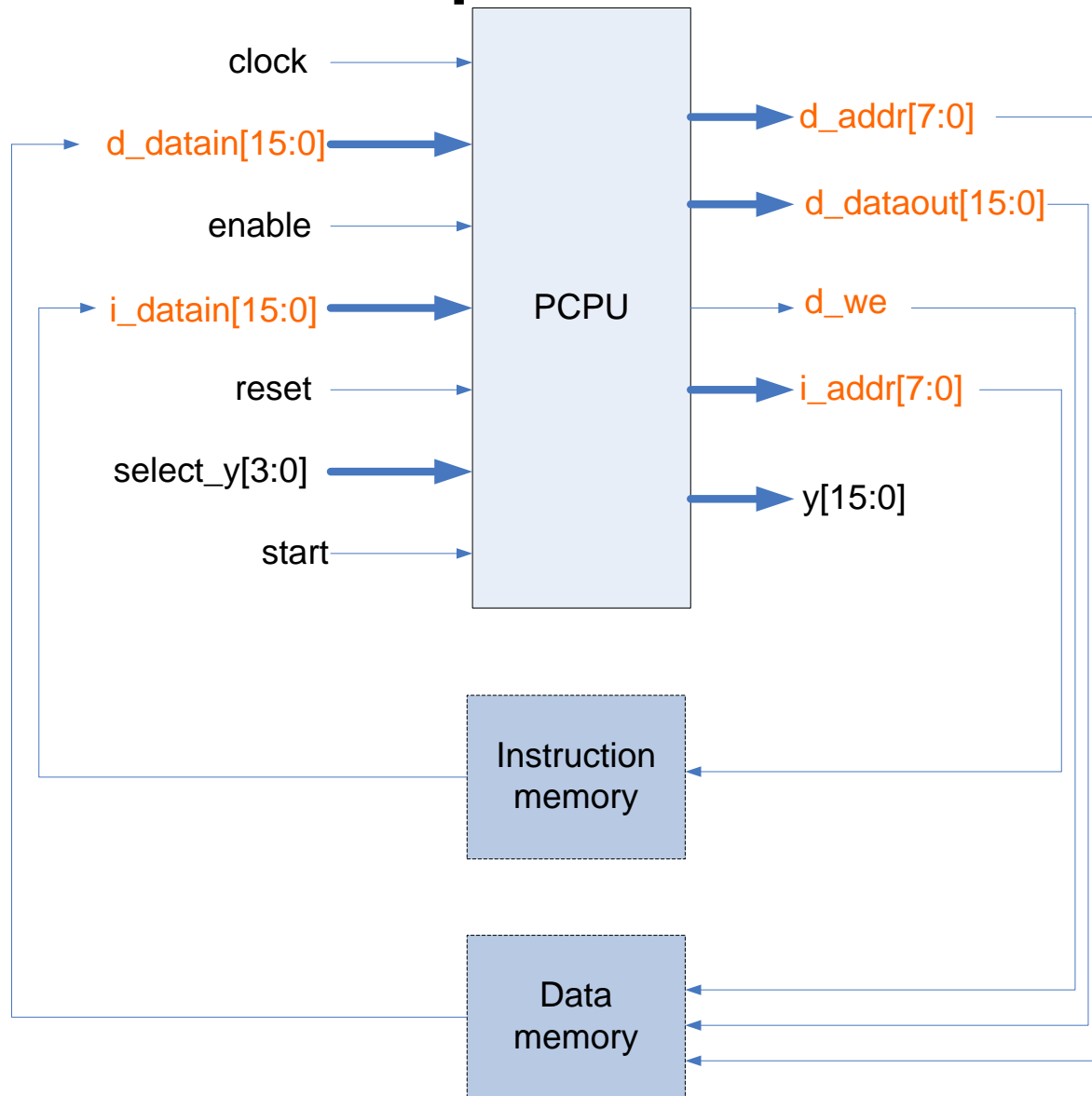

Storage


- Outside CPU core (SRAM, on-chip mem)
 - Instruction storage
 - Instruction memory ($2^5 \times 16b$)
 - Data storage
 - Data memory ($2^8 \times 16b$)
- Inside CPU core
 - Instruction storage
 - Stage instruction registers
 - id_ir(16b x 1), ex_ir (16b x 1), mem_ir (16b x 1), wb_ir (16b x 1)
 - Data storage
 - General registers
 - Storage for operand data ($2^3 \times 16b$)
 - Stage data registers
 - @ID: reg_A (16b x 1), reg_B (16b x 1), smdr (16b x 1),
 - @EX : reg_C (16b x 1), flag (1b x 3), dw (1b x 1), smdr1 (16b x 1),
 - @WB: reg_C1 (16b x 1)

CPU control

 

```
2  always @(posedge clock)
3  begin
4      if (!reset)
5          state <= `idle;
6      else
7          state <= next_state;
8      end
9
10 always @(*)
11 begin
12     case (state)
13     `idle :
14         if ((enable == 1'b1)
15             && (start == 1'b1))
16             next_state <= `exec;
17         else
18             next_state <= `idle;
19     `exec :
20         if ((enable == 1'b0)
21             || (wb_ir[15:11] == `HALT))
22             next_state <= `idle;
23         else
24             next_state <= `exec;
25     endcase
26 end
```

IF

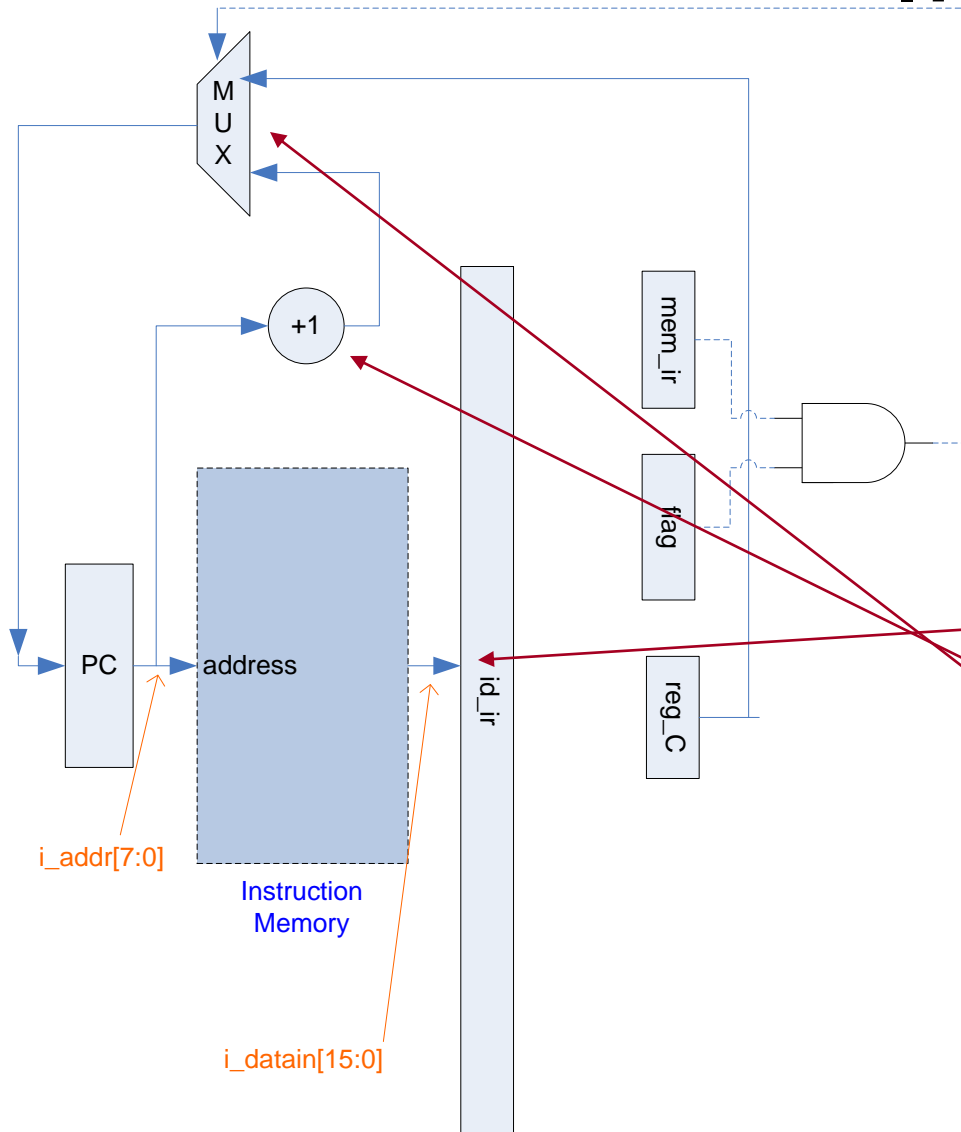

```

always @(posedge clock or negedge reset)
begin
    if (!reset)
    begin
        id_ir <= 16'b0000_0000_0000_0000;
        pc <= 8'0000_0000;
    end

    else if (state == `exec)
    begin
        id_ir <= i_datain;

        if((mem_ir[15:11] == `BZ)
            && (zf == 1'b1))
        || ((mem_ir[15:11] == `BN)
            && (nf == 1'b1)))
            pc <= reg_C[7:0];
        else
            pc <= pc + 1;
    end
end


```

ID


reg_A: 1st input operand of ALU, always gr[]

reg_B: 2nd input operand of ALU, gr[] or val

smdr: used only for STORE

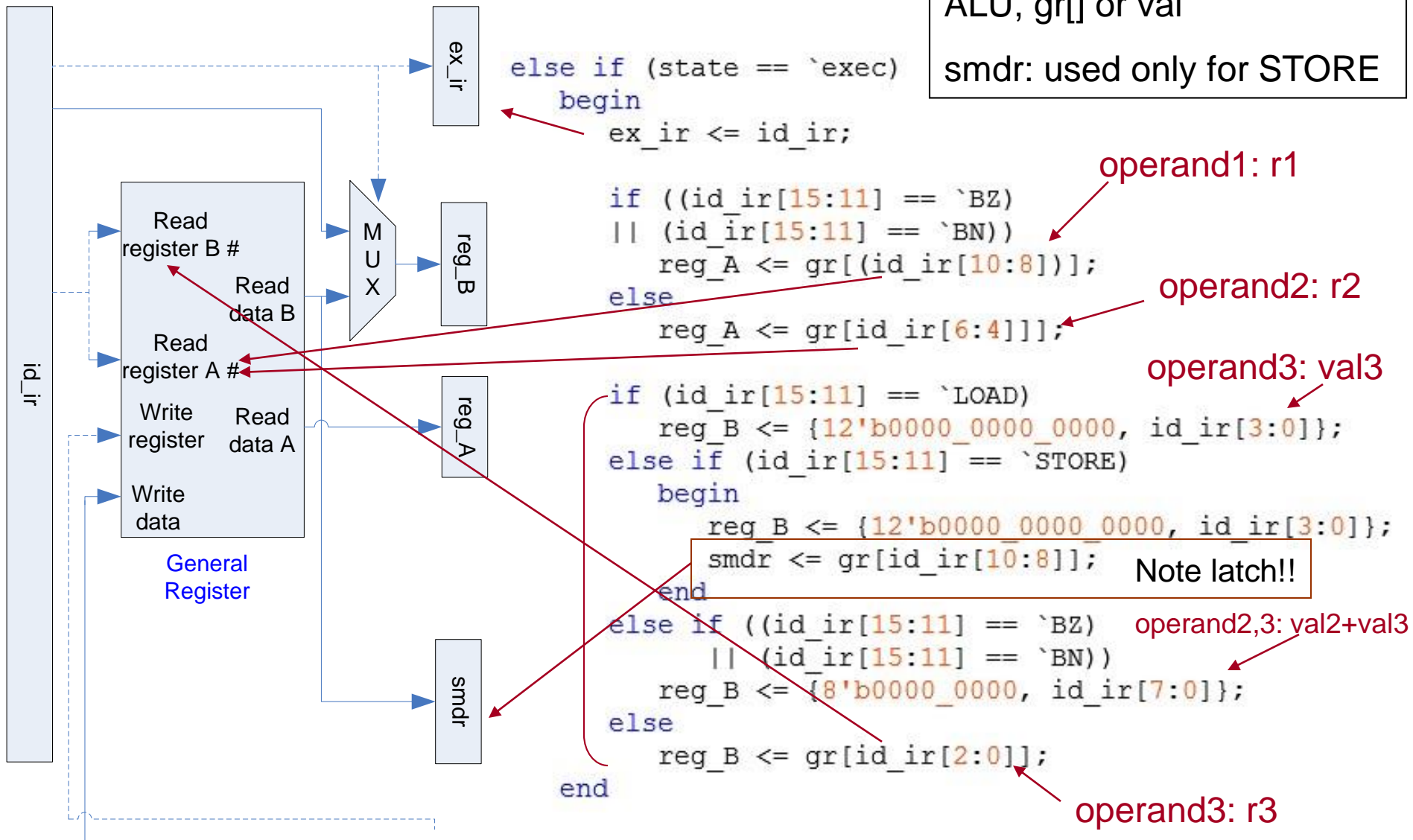

EX

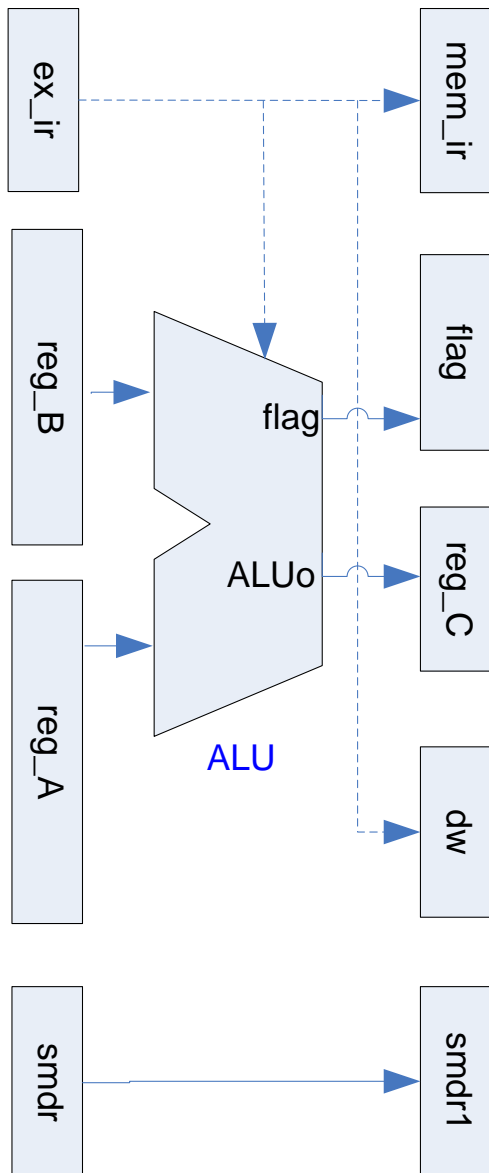

```


else if (state == `exec)
begin
    mem_ir <= ex_ir;
    reg_C <= ALUo;

    if ((ex_ir[15:11] == `ADD)
        || (ex_ir[15:11] == `CMP))
    begin
        if (ALUo == 16'b0000_0000_0000_0000)
            zf <= 1'b1;
        else
            zf <= 1'b0;
        begin
            if (ALUo[15] == 1'b1)
                nf <= 1'b1;
            else
                nf <= 1'b0;
        end
    end
    if (ex_ir[15:11] == `STORE)
    begin
        dw <= 1'b1;
        smdr1 <= smdr;
    end
    else
        dw <= 1'b0;
end
end

```

Note
latch !

MEM

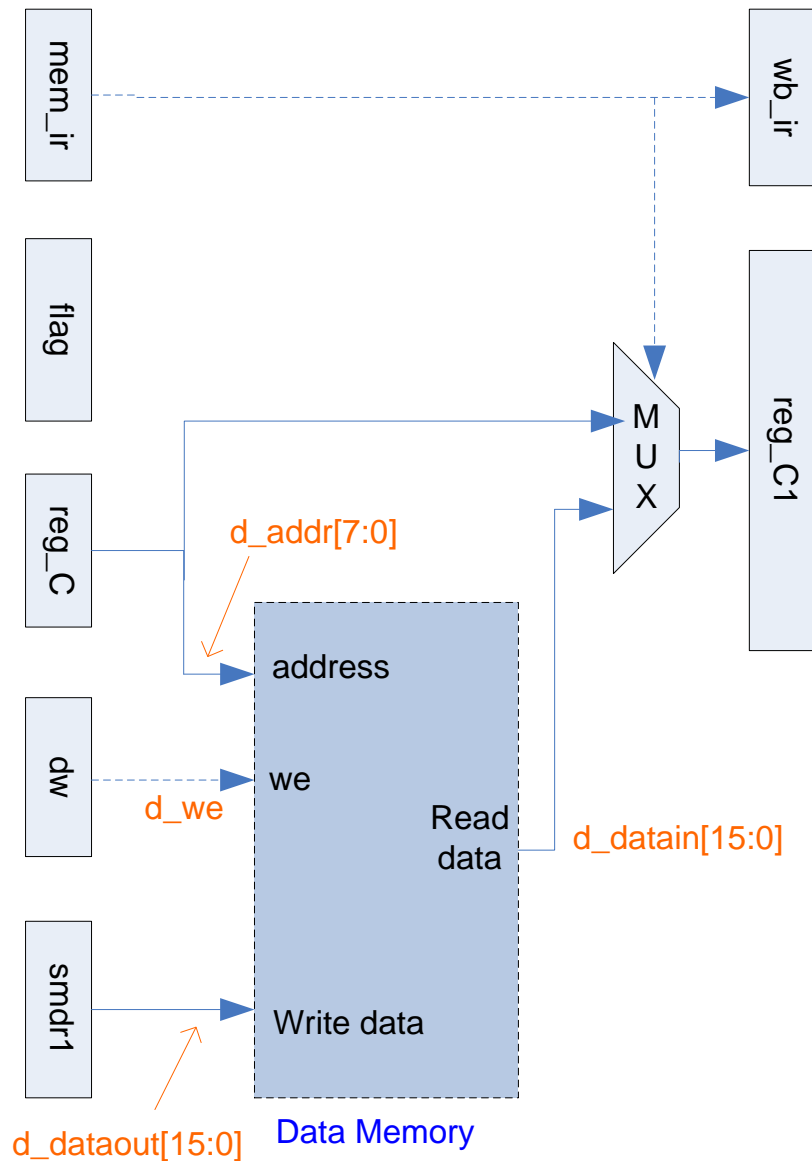


```

else if (state == `exec)
begin
    wb_ir <= mem_ir;

    if (mem_ir[15:11] == `LOAD)
        reg_C1 <= d_datain;
    else
        reg_C1 <= reg_C;
end
    
```

WB

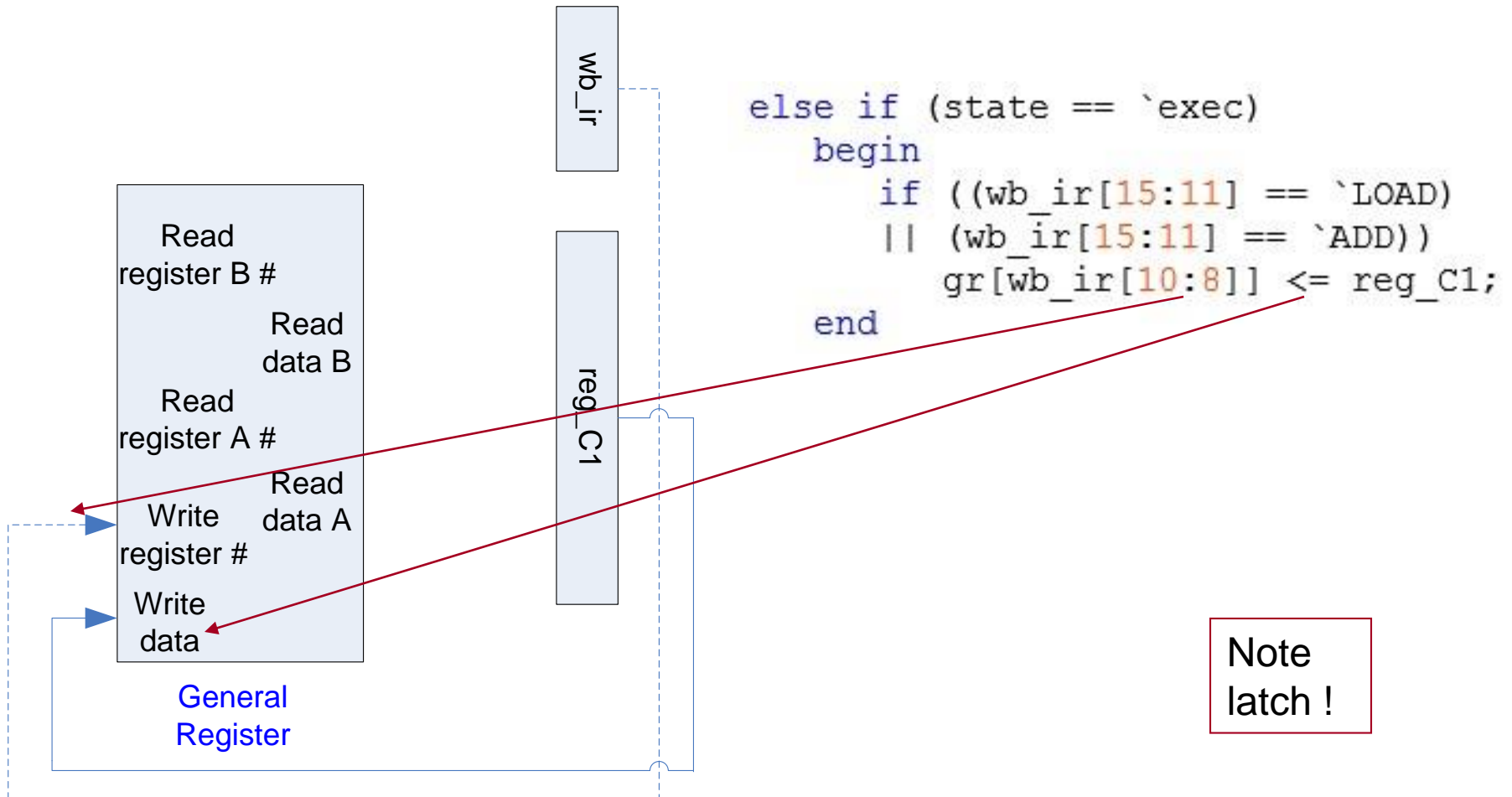

Example of test pattern (texture simulation)

```
$display("pc:      id_ir      :reg_A:reg_B:reg_C:da:dd:  :w:reC1:gr1 :gr2 : gr3");
$monitor("%h:%b:%h:%h:%h:%h:%h:%b:%h:%h:%h:%h",
    pcpcu.pc, pcpcu.id_ir, pcpcu.reg_A, pcpcu.reg_B, pcpcu.reg_C,
    d_addr, d_dataout, d_we, pcpcu.reg_C1, pcpcu.gr[1], pcpcu.gr[2], pcpcu.gr[3]);

enable <= 1; start <= 0; i_datain <= 0; d_datain <= 0; select_y <= 0;

#10 reset <= 0;
#10 reset <= 1;
#10 enable <= 1;
#10 start <= 1;
#10 start <= 0;
    i_datain <= {\`LOAD, \`gr1, 1'b0, \`gr0, 4'b0000};
#10 i_datain <= {\`LOAD, \`gr2, 1'b0, \`gr0, 4'b0001};
#10 i_datain <= {\`NOP, 11'b000_0000_0000};
#10 i_datain <= {\`NOP, 11'b000_0000_0000};
    d_datain <= 16'h00AB; // 3 clk later from LOAD
#10 i_datain <= {\`NOP, 11'b000_0000_0000};
    d_datain <= 16'h3C00; // 3 clk later from LOAD
#10 i_datain <= {\`ADD, \`gr3, 1'b0, \`gr1, 1'b0, \`gr2};
#10 i_datain <= {\`NOP, 11'b000_0000_0000};
#10 i_datain <= {\`NOP, 11'b000_0000_0000};
#10 i_datain <= {\`NOP, 11'b000_0000_0000};
#10 i_datain <= {\`STORE, \`gr3, 1'b0, \`gr0, 4'b0010};
#10 i_datain <= {\`HALT, 11'b000_0000_0000};
```



```
LOAD gr1, gr0, 0
LOAD gr2, gr0, 1
NOP
NOP
NOP
NOP
ADD gr3, gr1, gr2
NOP
NOP
NOP
NOP
STORE gr3, gr0, 2
HALT
```

Simulation results (texture)

- Please test by yourself, and analyse it

pc: id_ir :reg_A:reg_B:reg_C:da:dd: :w:reC1:gr1 :gr2 : gr3

Finished circuit initialization process.

xx:xxxxxxxxxxxxxxxxxxxx:xxxx:xxxx:xxxx:xx:xxxx:x:xxxx:xxxx:xxxx:xxxx

00:0000000000000000:0000:0000:0000:xx:xxxx:x:0000:0000:0000:0000

01:0001000100000000:0000:0000:xxxx:xx:xxxx:x:0000:0000:0000:0000

02:0001001000000001:0000:0000:xxxx:xx:xxxx:x:xxxx:0000:0000:0000

03:0000000000000000:0000:0001:0000:xx:xxxx:x:xxxx:0000:0000:0000

04:0000000000000000:0000:0000:0001:xx:xxxx:x:00ab:0000:0000:0000

05:0000000000000000:0000:0000:0001:xx:xxxx:x:3c00:00ab:0000:0000

06:0100001100010010:0000:0000:0001:xx:xxxx:x:0001:00ab:3c00:0000

07:0000000000000000:00ab:3c00:0001:xx:xxxx:x:0001:00ab:3c00:0000

08:0000000000000000:0000:0000:3cab:xx:xxxx:x:0001:00ab:3c00:0000

09:0000000000000000:0000:0000:3cab:xx:xxxx:x:3cab:00ab:3c00:0000

0a:0001101100000010:0000:0000:3cab:xx:xxxx:x:3cab:00ab:3c00:3cab

0b:0000100000000000:0000:0002:3cab:xx:xxxx:x:3cab:00ab:3c00:3cab

0c:0000100000000000:0000:0000:0002:xx:xxxx:x:3cab:00ab:3c00:3cab

0d:0000100000000000:0000:0000:0002:xx:xxxx:x:0002:00ab:3c00:3cab


0e:0000100000000000:0000:0000:0002:xx:xxxx:x:0002:00ab:3c00:3cab

0f:0000100000000000:0000:0000:0002:xx:xxxx:x:0002:00ab:3c00:3cab

LOAD gr1, gr0, 0
LOAD gr2, gr0, 1
NOP
NOP
NOP
ADD gr3, gr1, gr2
NOP
NOP
NOP
STORE gr3, gr0, 2
HALT

Board evaluation

System_on_Board

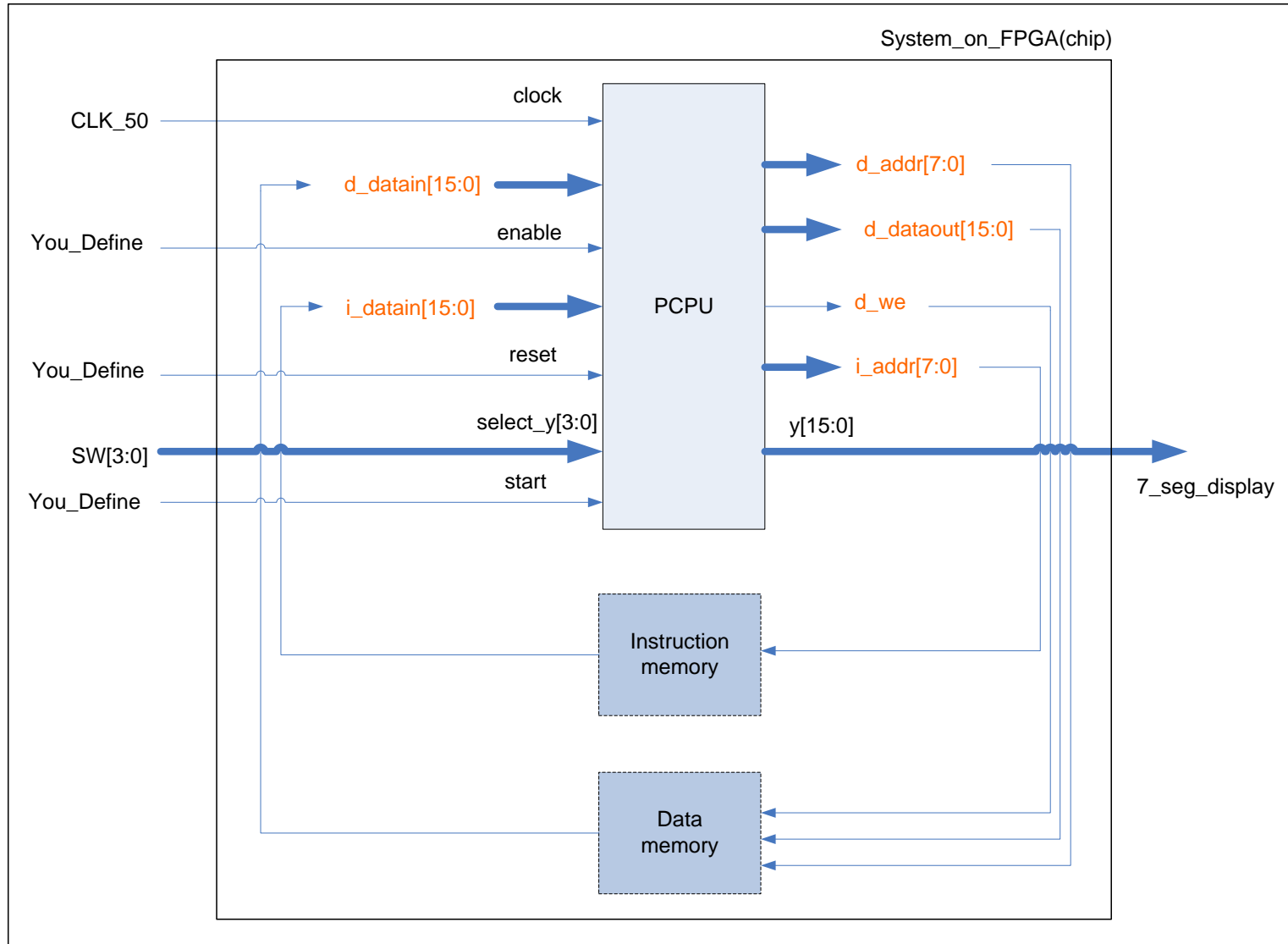

Memory implementation

- Write verilog by yourself
- Use **Core_Generate(ISE)/IP_Catalog(vivado)** to generate IP
 - Get the verilog built in
 - Memory initialization file (for testbench)
 - .mif (altera)
 - .coe (xilinx)
 - All available via course website
 - Study more on how to generate IP and use IP by website
 - eg., <http://xilinx.eetop.cn/?action-viewnews-itemid-2516>

Concept behind

- System on Chip
 - SOC
- From SOB to SOC
 - System on board to system on chip
- SOC

- Processor
 - ARM/DSP/MIPS/X86
 - Program with C/C++
- Memory
- FPGA/ASIC
 - Your own verilog




SOPC: (P: programmable)

Newly FPGA, the state-of-art all programmable device, can cover everything with low cost solution, and acceptable performance,

- Therefore, software and hardware division is a problem
 - New design methodology
 - SW/HW Co-design
 - Key of embedded system design

Embedded System Design

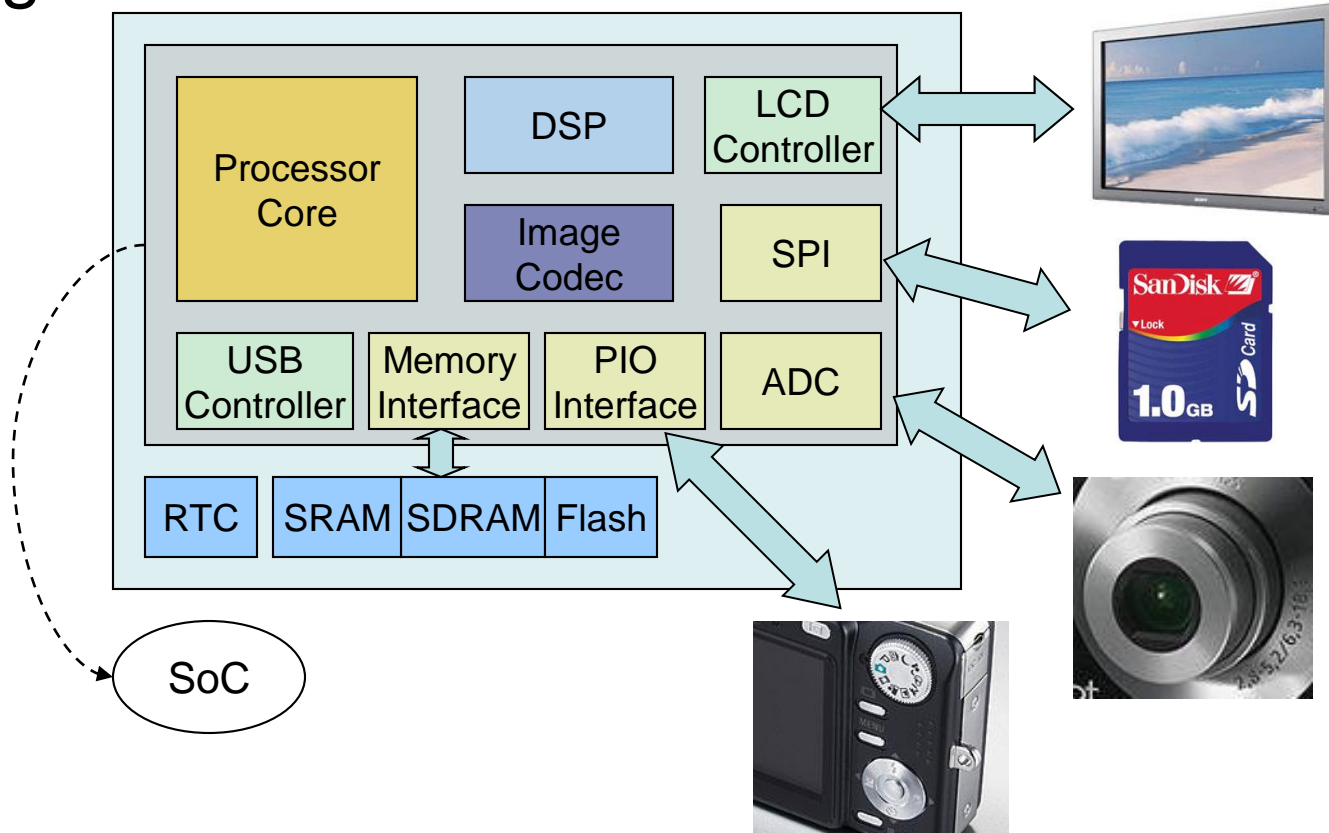- Example: Digital camera hardware block diagram



Labs

- 1, Complete the designs above
 - Complete the verilog with variable declarations
 - Simulate by the test pattern (texture simulation), (not board verification)
- 2, Add more to your verilog
 - Complete the left operations other than * ones
 - LDIH, ADDI, ADDC, ...
 - Add flag register
 - CF
 - Add your original operations
 - You can add up to 5 ops with unused codes: 10011, 10100, 10101, 10110, 10111.
 - Design you own test patterns
- 3, Board verification
- Submit your report due to May 15th
 - Your own operation set description (like the table in slide#7/8/9), verilog, testbench
 - snapshot of simulation (texture only), RTL snapshots, Board running snapshot, design report (timing/area/power).
 - Impression (感想) on this project

Further projects

---Hazards

Hazards


- Situations that prevent starting the next instruction in the next cycle
- Structure hazards
 - A required resource is busy
- Data hazard
 - Need to wait for previous instruction to complete its data read/write
- Control hazard
 - Deciding on control action depends on previous instruction

Structure Hazards

- Conflict for use of a resource
- In X86 (by intel) pipeline with a single memory
 - Load/store requires data access
 - Instruction fetch would have to *stall* for that cycle
 - Would cause a pipeline “bubble”
 - So called **von Neumann structure**
- In ARM/MIPS pipeline
 - separate instruction/data caches
 - So called **Harvard structure**

Data Hazards

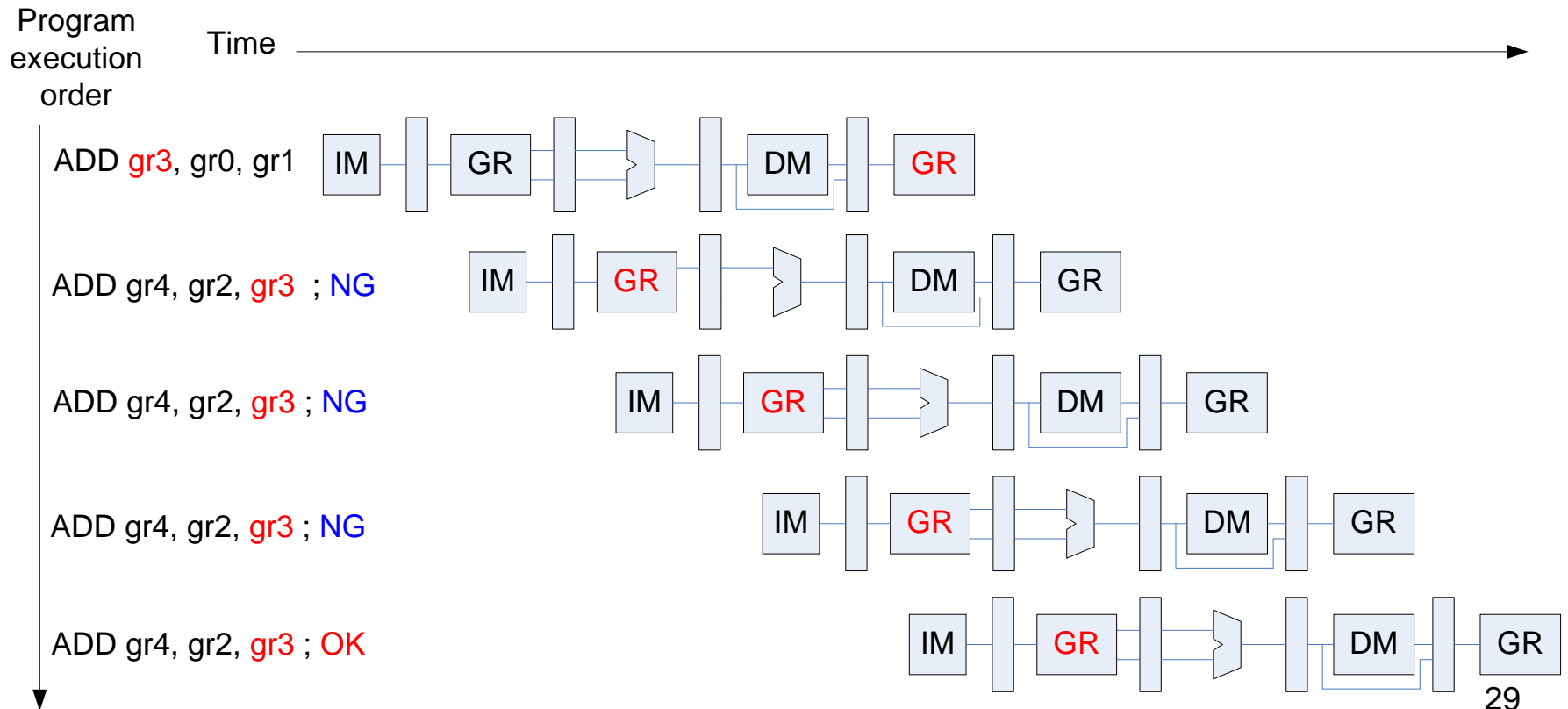
- An instruction depends on completion of data access by a previous instruction



Solution

- Software
 - Insert 3 NOPs
- Hardware
 - Data forward
 - For arithmetic op
 - Data forward & Stall
 - For LOAD


Data forwarding

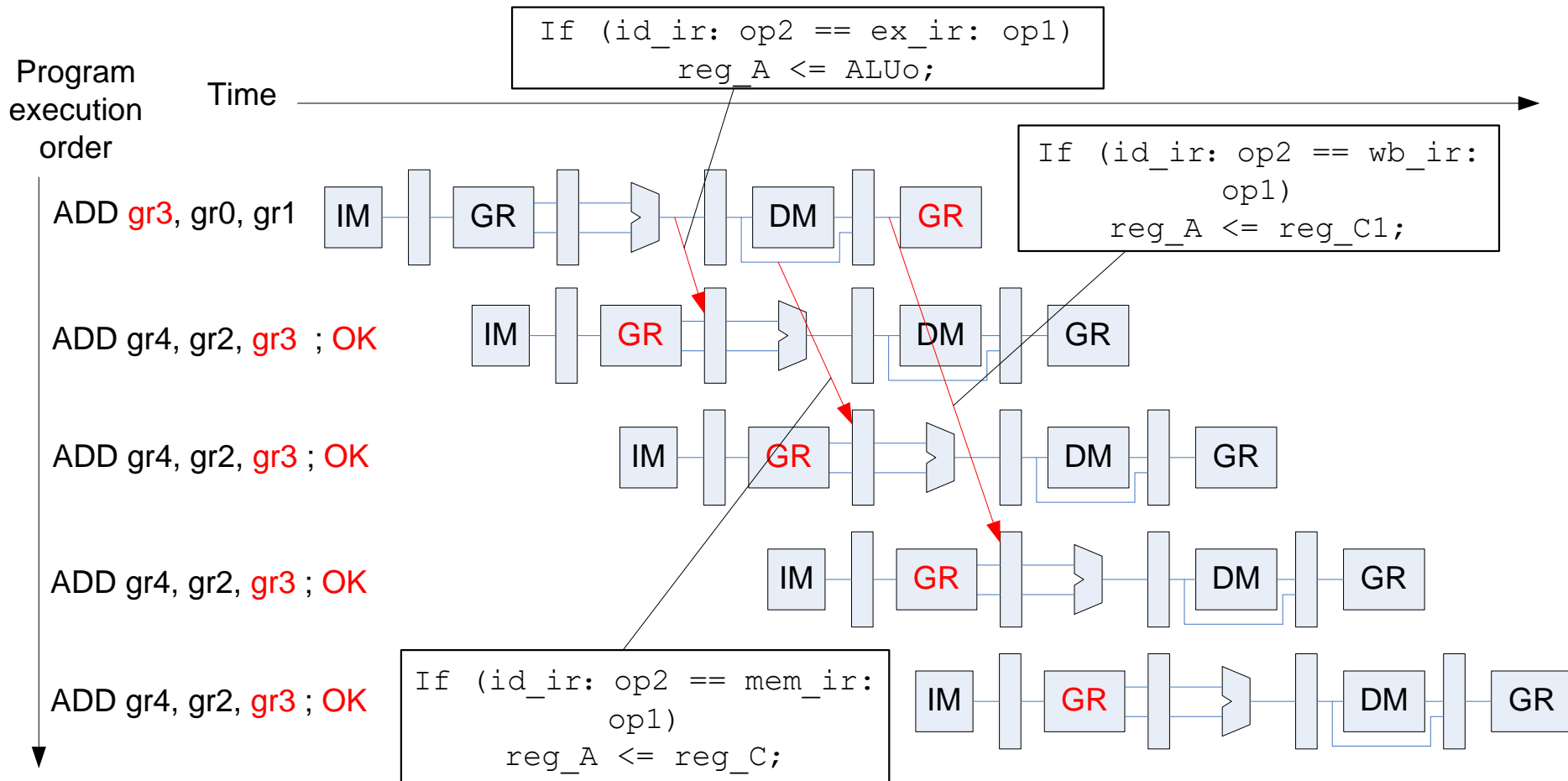

Data forwarding happens in ID stage,
always check *id_ir* to decide *reg_A/B*

Can't always forwarding

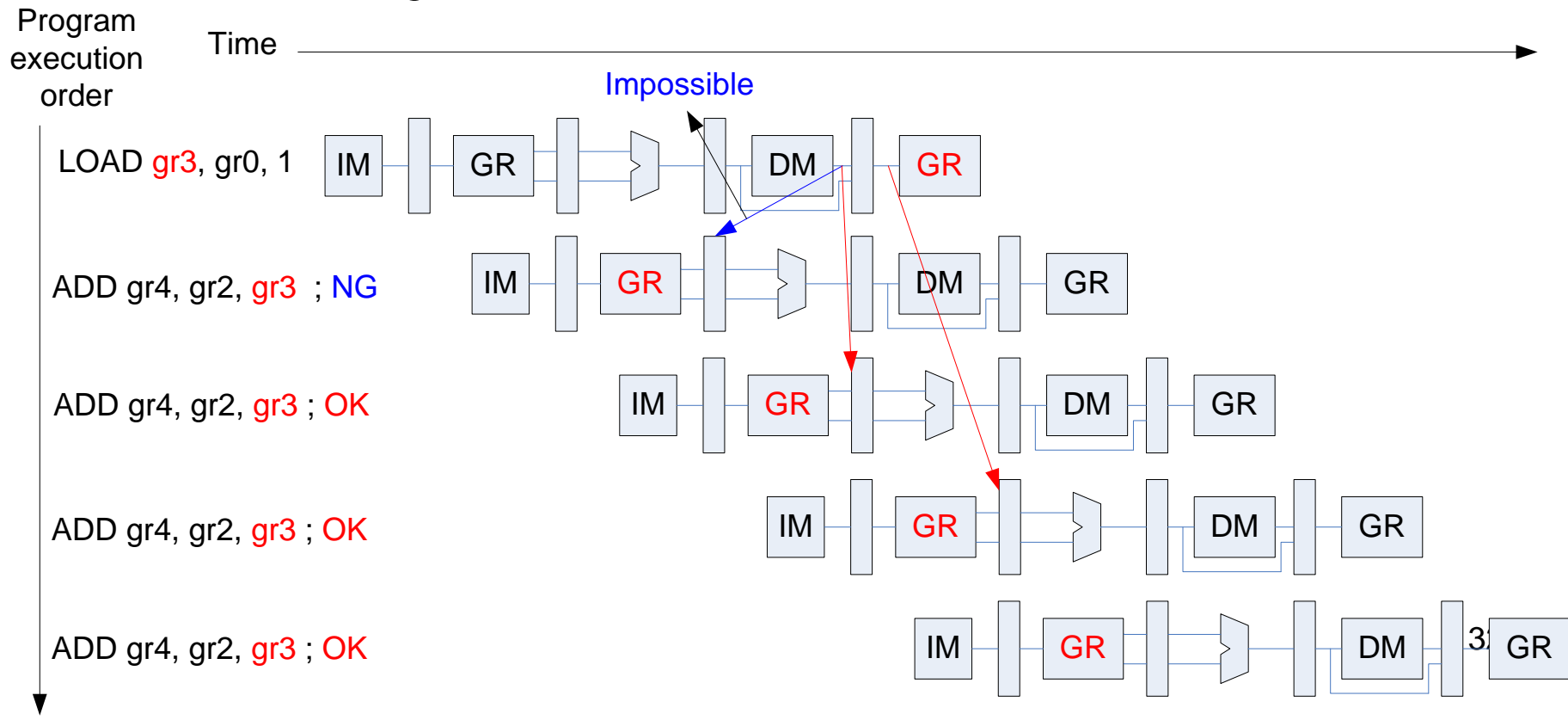- “LOAD” can still cause hazard
 - since data was accessed from data memory
 - after reg_C




Solution

- Software
 - Insert 3 NOPs
- Hardware
 - Joint usage of Data forwarding & Stall
 - Data forwarding to solve 2nd and 3rd NOPs
 - Stall to solve 1st NOP

Stall

- Stall the pipeline by keeping an instruction in the same stage

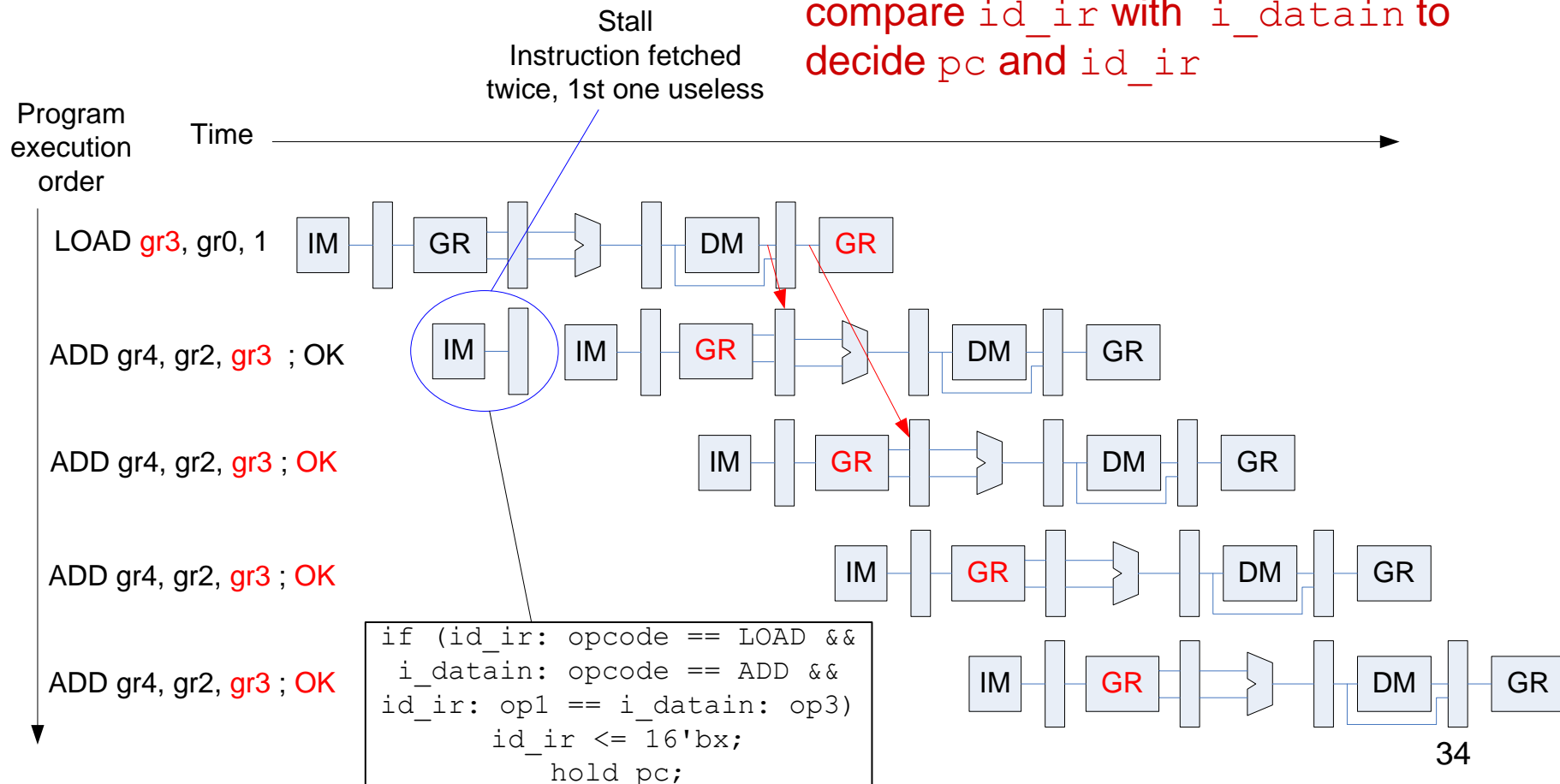Stall happens in IF stage, always compare `id_ir` with `i_datain` to decide `pc` and `id_ir`



Control Hazard

- When CPU decide to branch, other instructions are still in pipeline!!
 - During the time from branch instruction fetch to branch address generate (from IF to ID to EX to MEM, 3 stages),
 - the 3 instructions followed by branch are in pipeline.
 - The computing results by them are useless
 - Should be flushed
 - or will impact the following instructions computing

Solution

- Software
 - Insert 3 NOPs
 - Insert independent operations
- Hardware
 - Flushing...

Labs

- 1, Finish both the data and control hazard HW solution design by Verilog
- 2, pass the 复杂指令测试 show in the website.
- 3, Board verification (including 复杂指令测试)
- Submit your report due to Jun 29th
 - Your own verilog, testbench
 - snapshot of simulation (texture only), RTL snapshots, Board running snapshot, design report (timing/area/power).
 - Impression (感想) on this project

Summary

- Hazard
 - Structure
 - Data
 - Arithmetic
 - Software solution
 - » NOP
 - Hardware solution
 - » Data forwarding
 - LOAD
 - Software solution
 - » NOP
 - Hardware solution
 - » Stall+Data forwarding
 - Control
 - Software solution
 - » NOP
 - » Independent operation
 - Hardware solution
 - » Flushing